

# More bits, circuits, adders (From the last class)

---

## CS 2130: Computer Systems and Organization 1

**Xinyao Yi** Ph.D.  
Assistant Professor

## Announcements

---

- Homework 1 due Monday

## Adder

---

Can we use this in parallel to add multi-bit numbers?

What is missing?



Consider:

$$\begin{array}{r} \overset{1}{1}1 \\ +01 \\ \hline 100 \end{array}$$

Since I have a carry-in  
2 inputs  $\rightarrow$  3-inputs adder.


# 3-input Adder

Add 3 1-bit numbers:  $a$ ,  $b$ ,  $c$

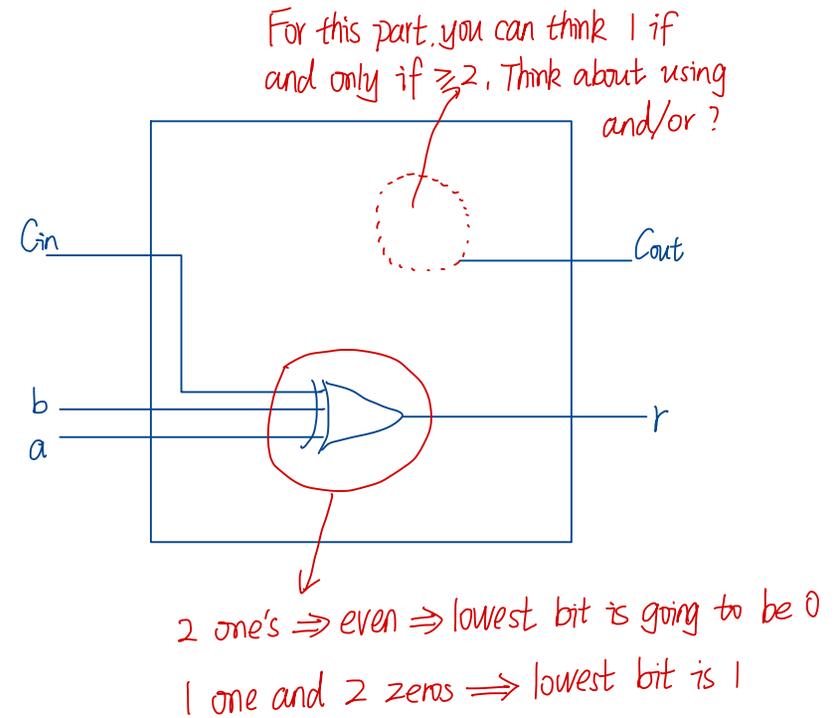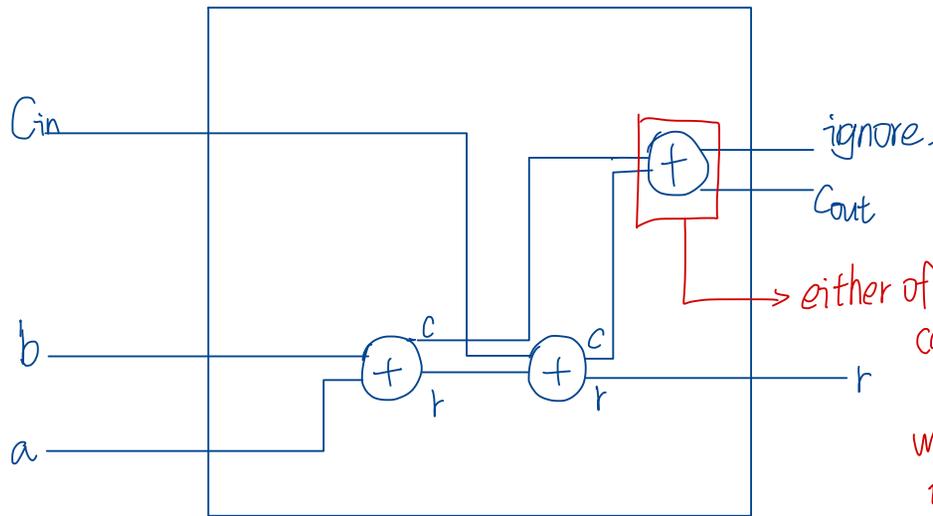
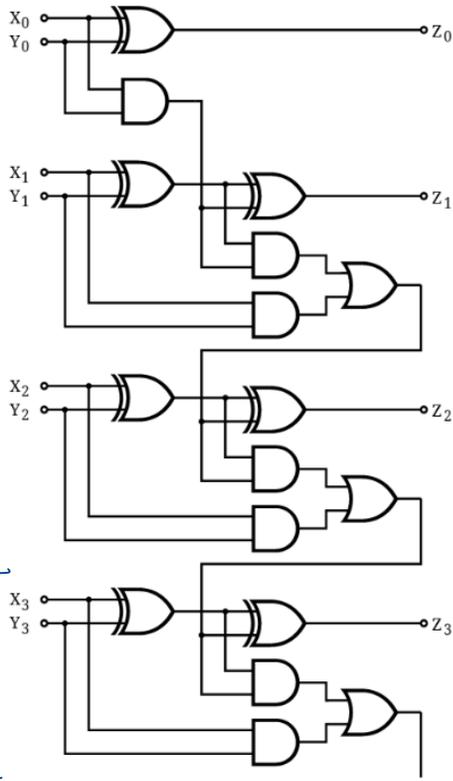
# Ripple-Carry Adder

$$\begin{array}{r} X_3 X_2 X_1 X_0 \\ + Y_3 Y_2 Y_1 Y_0 \\ \hline Z_3 Z_2 Z_1 Z_0 \end{array}$$



repeat if  
more bits

verify:

unsigned.

$$\begin{array}{r} 1111 (15) \\ + 1111 (15) \\ \hline \end{array}$$

drop ← ① 1110 (14) ← overflow!


signed?

$$\begin{array}{r} 1111 (-1) \\ + 1111 (-1) \\ \hline 1110 (-2) \end{array}$$


works!

## Ripple-Carry Adder: Lowest-order Bit


(one bit, 2 inputs adder)

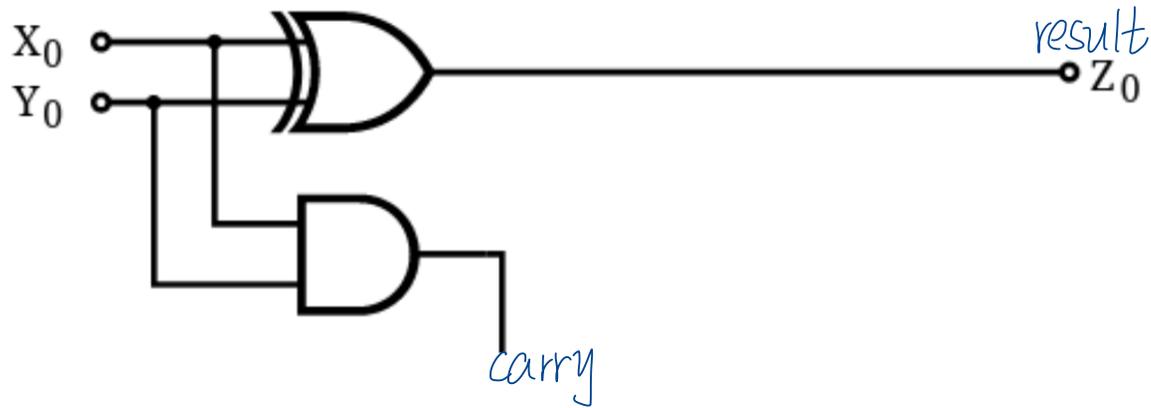

## Ripple-Carry Adder: In General

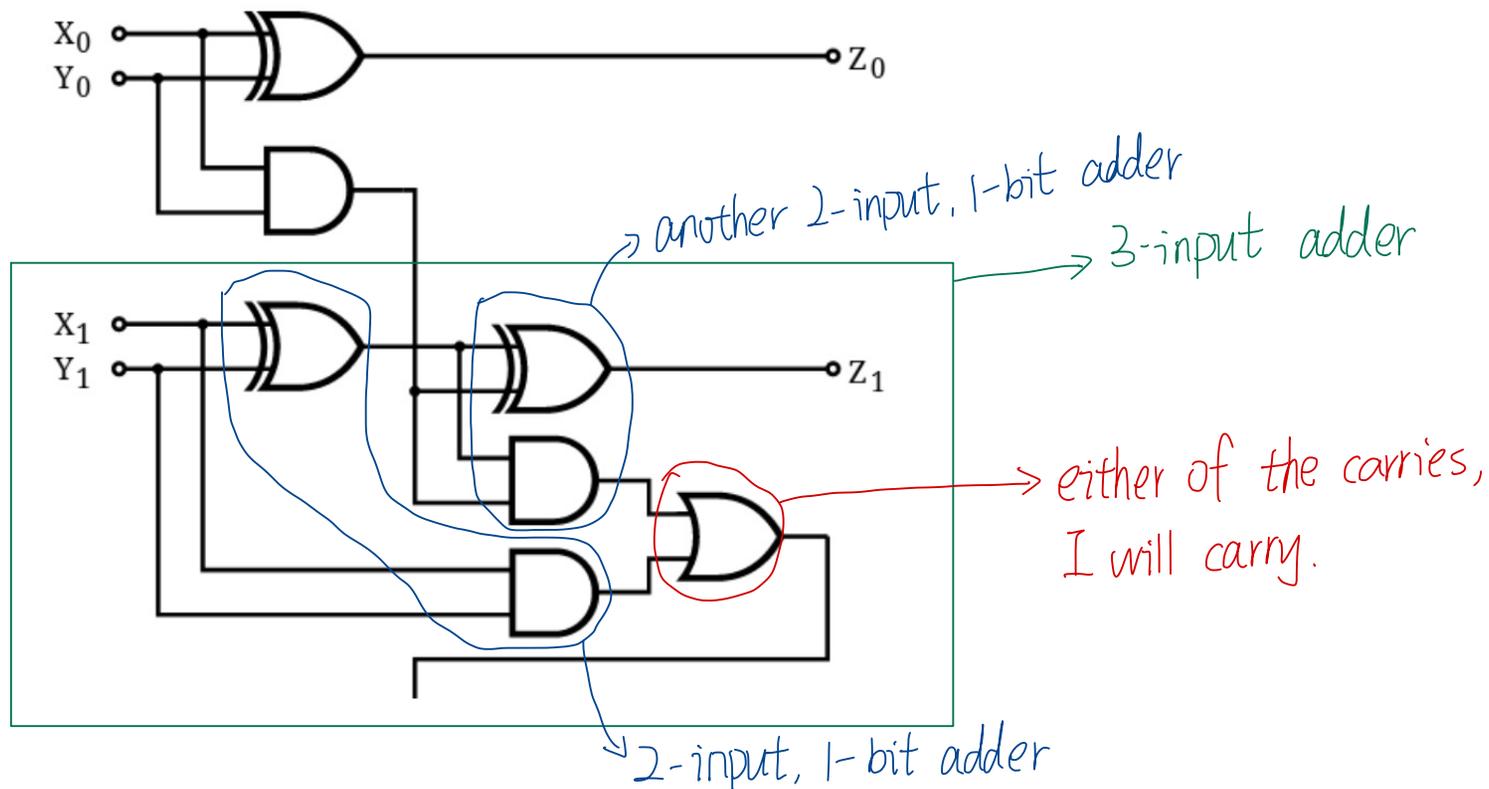

## Ripple-Carry Adder: In General

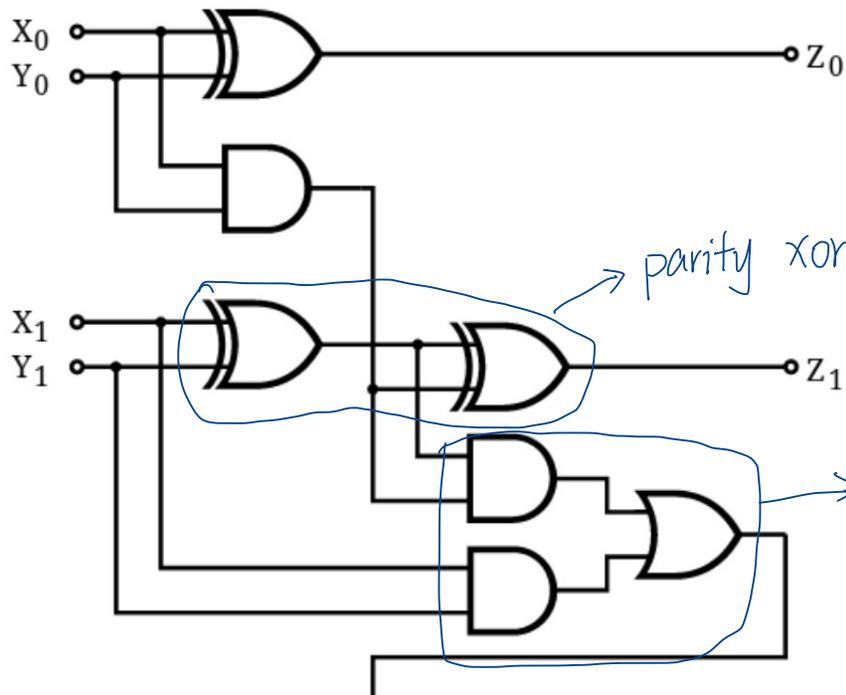

carry  
(if I have at least 2 one's,  
I will carry).


# Clocks, Registers

---

## CS 2130: Computer Systems and Organization 1

**Xinyao Yi** Ph.D.  
Assistant Professor


## What does this circuit do?

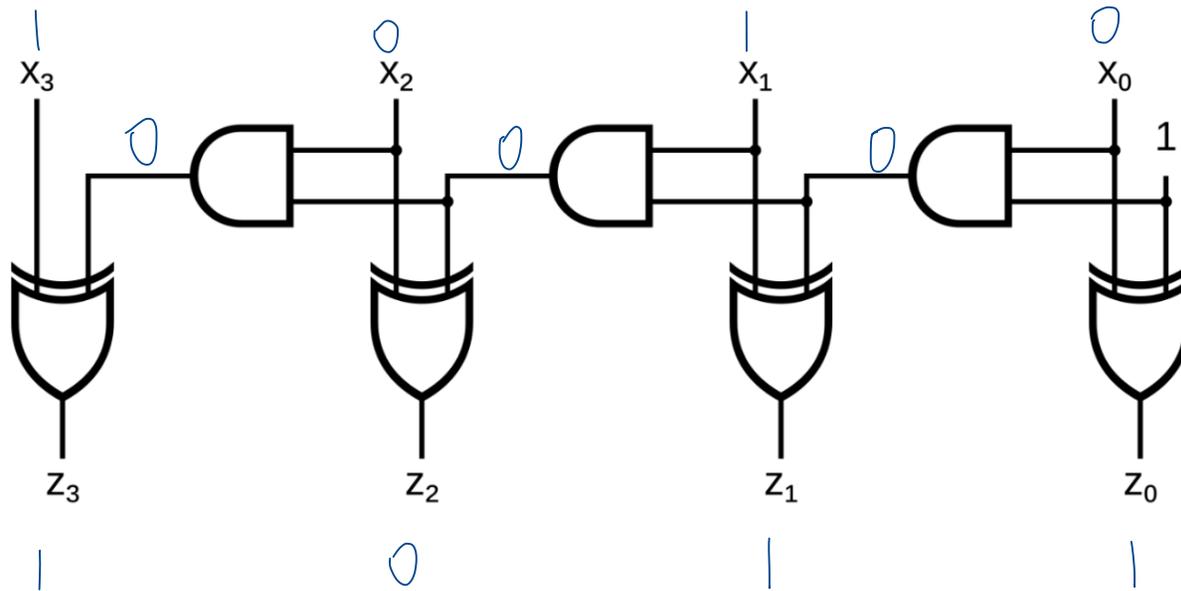


*It adds 1 !*

# Increment Circuit

*I want a counter.*

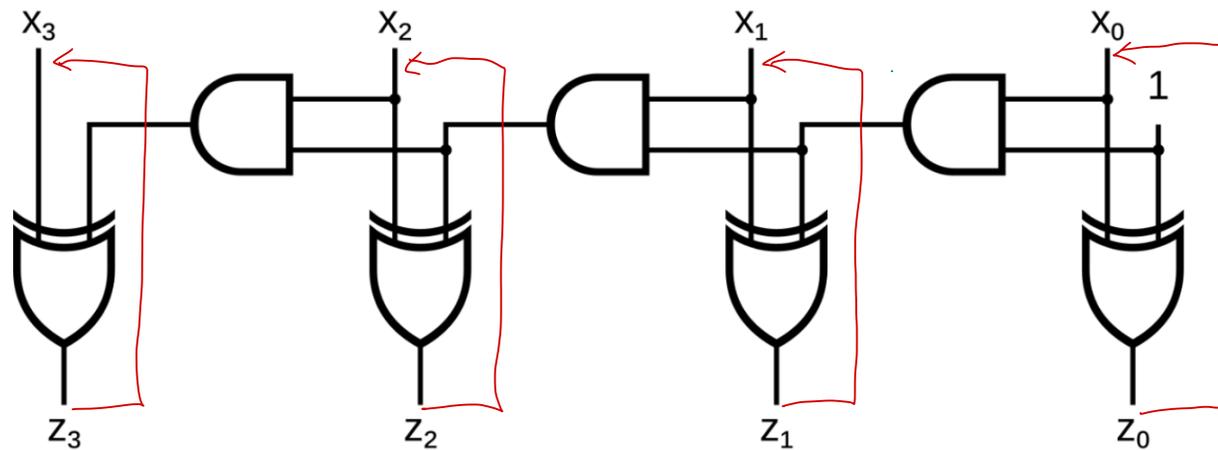

*Idea:*

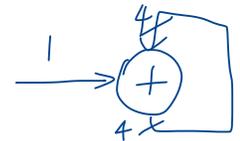



*out put a one, then  
feed itself back, then  
I can count.*

*glitch happens!*

*I want to remember the current value.  
use it as the input for the next calculation.*

## Gate Delay


What happens when I change my input?

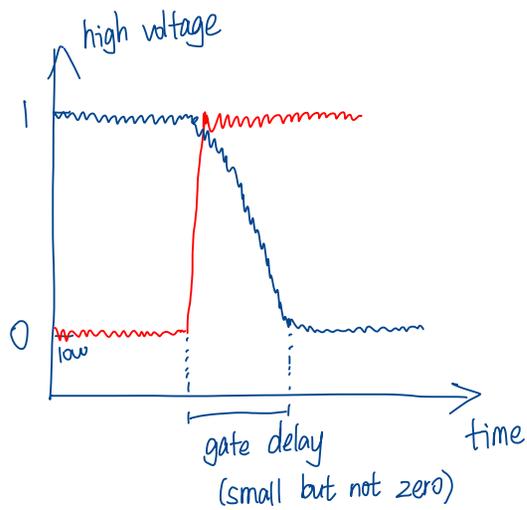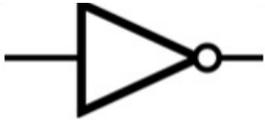

My input could change instantly,  
but the output does not!


## Building a Counter

So what we want to do:

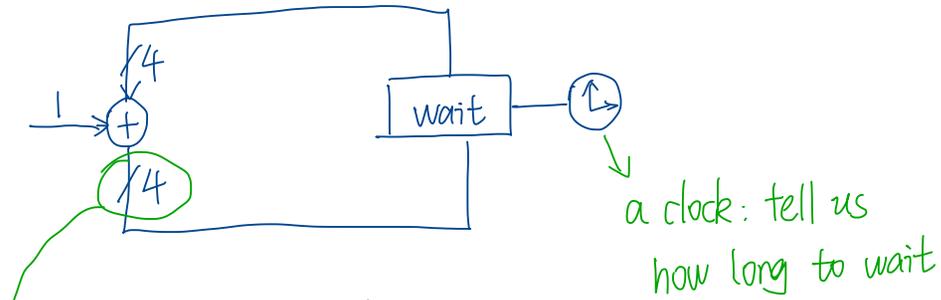

↓  
 a bundle of wires  
 ↓  
 no need to draw all wires


a register:

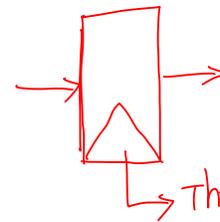

It is a memory element.

↳ This triangle is the symbol of a clock.


# 1-bit Register Circuit

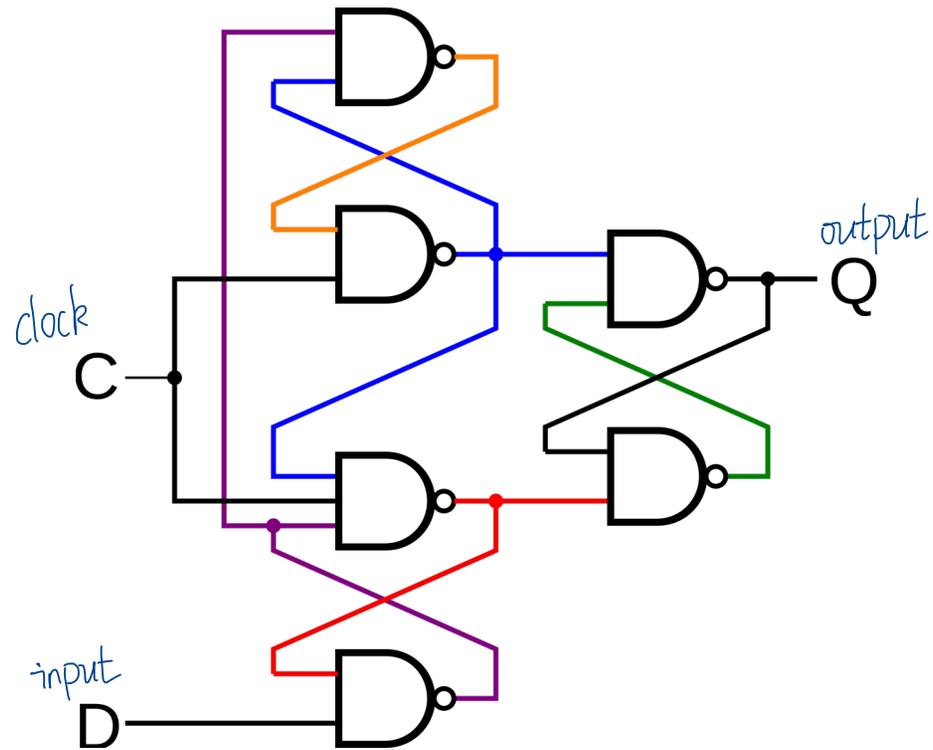

$\Rightarrow D_0$  — NAND gate

0	0	1
0	1	1
1	0	1
1	1	0

## 1-bit Register Circuit

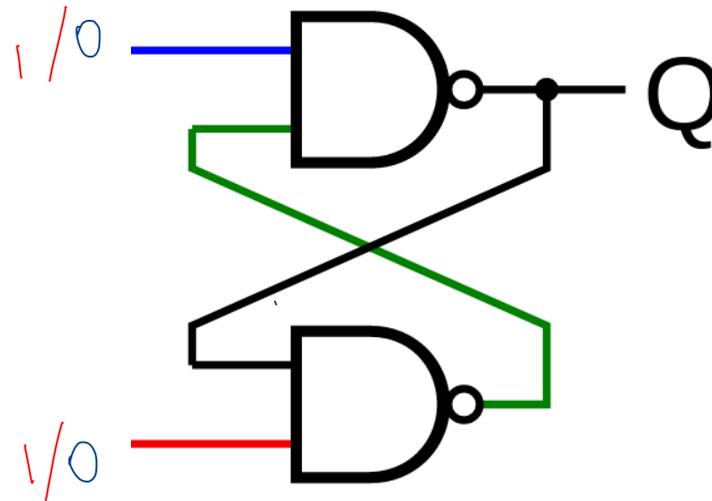

if my inputs are zeros:  
make Q change from 0→1  
or keep 1.

if my inputs are ones:  
stay the values.

# 1-bit Register Circuit

*D flip-flop.*


When the clock is low:  
The register monitors the input D, but it does not immediately update Q.

On the rising edge of the clock: The register samples the value of D and immediately updates Q.

At all other times: Even if D changes rapidly, Q remains unchanged until the next rising edge.

*Clock:*  
it is going to force other circuit either keep the value or change it


*input*

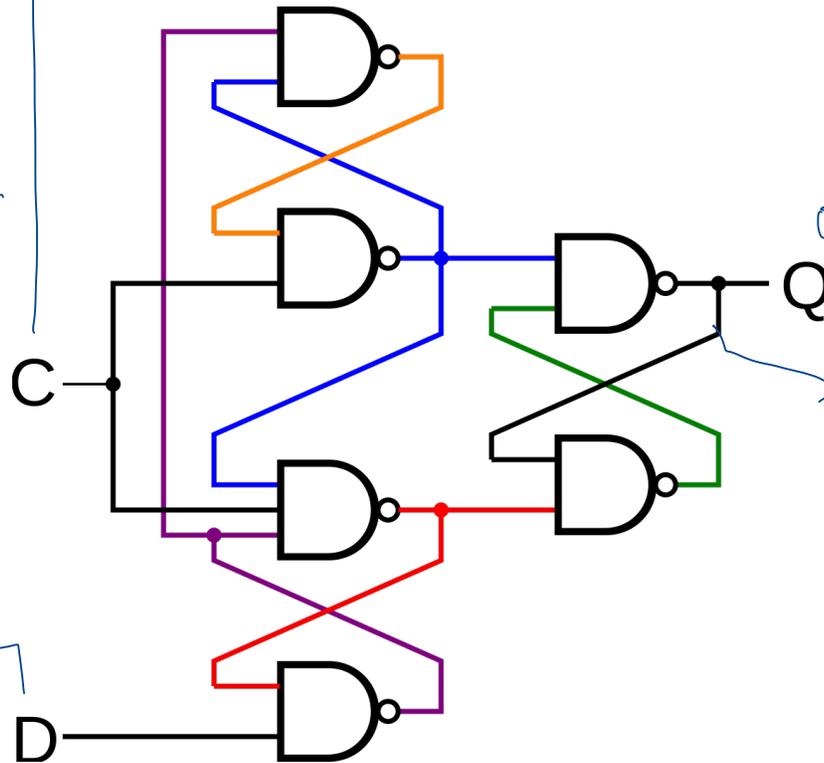


*output.*

*my "store" when I'm thinking about it. keeping track of that value.*


## Building a Counter

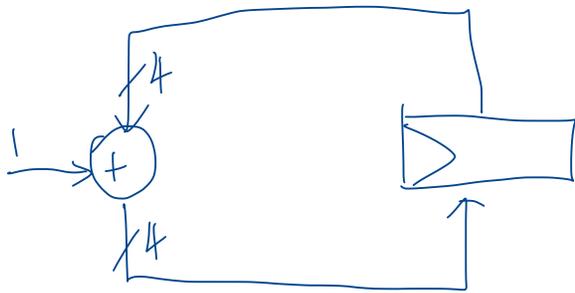

four-bit register:

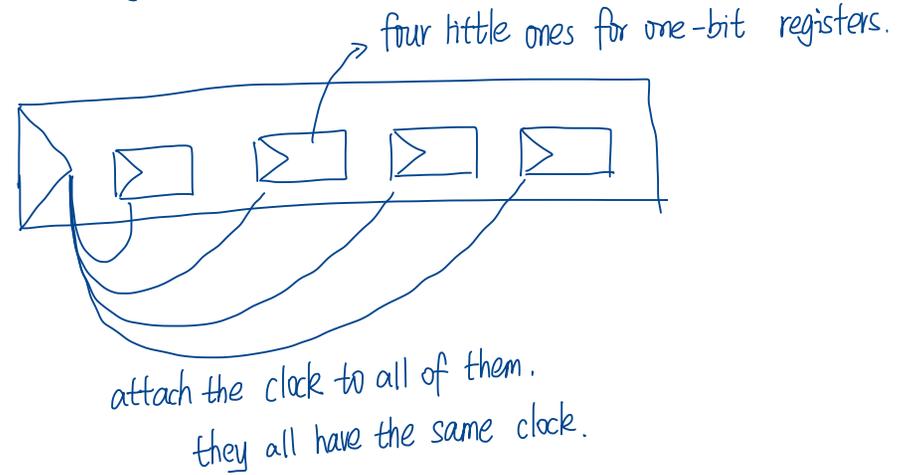

## Another Counter

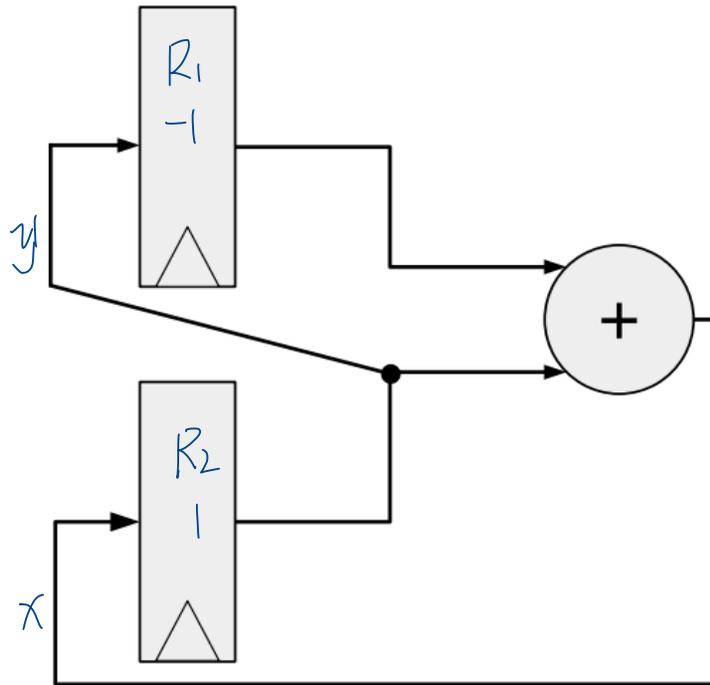

clock	$R_1$	$R_2$	$x$	$y$
0	-1	1	0	1
1	1	0	1	0
2	0	1	1	1
3	1	1	2	1
4	1	2	3	2
5			5	3

$x$ : Fibonacci Sequence.

## Another Counter

